

[과제 4] 4bit x 4bit = 8bit Multiplier(Signed Magnitude) 설계

```
//과제 4
//이름: 이창민
//학번:2019043890
//융합전자공학부

// Code your design here
module mul8_sign (

    input signed [3:0] a, b,
    input clk, rstn, start,
    output reg [7:0] result,
    output reg done
);

    localparam IDLE = 3'b000, //0
               START = 3'b001, //1
               LSB = 3'b010, //2
               ADD = 3'b011, //3
               SHIFT = 3'b100, //4
               DONE = 3'b101; //5

    reg [7:0] r_multiplicand, r_product;
    reg [3:0] r_multiplier;
    reg [2:0] r_state,next_state;
    reg [1:0] r_count;
    reg sign;

    always @(posedge clk, negedge rstn) begin
        if (!rstn) r_state <= IDLE;
        else r_state<=next_state;
    end
    always @(*) begin
        case(r_state)
            IDLE:
                begin
                    if (start) begin
                        next_state = START;
                    end
                    else begin
                        next_state = IDLE;
                    end
                end
            START:
                begin
                    next_state=LSB;
                end
        endcase
    end
```

```

        end
    LSB:
        begin
            if(r_multiplier[0]) next_state = ADD;
            else next_state = SHIFT;
        end
    ADD:
        begin
            next_state = SHIFT;
        end
    SHIFT:
        begin
            if(r_count != 0)next_state=LSB;
            else next_state = DONE;
        end
    DONE:
        begin
            next_state= IDLE;
        end
    default:
        begin
            next_state= IDLE;
        end
    endcase
end
always @(posedge clk, negedge rstn) begin
    if (!rstn) begin
        r_multiplicand <= 0;
        r_multiplier <= 0;
        r_product <= 0;
        r_count <= 4;
        result <= 0;
        done <= 0;
    end
    else begin
        case (next_state)
            IDLE:
                begin
                    r_multiplicand <= 0;
                    r_multiplier <= 0;
                    r_product <= 0;
                    r_count <= 4;
                    result <= 0;
                    done <= 0;
                end
            START:
                begin

```

```

    if (a[3] == 1) begin //음수인지 체크
        r_multiplicand <= ~a + 1;
    end
    else begin
        r_multiplicand <= {4'b0000, a};
    end

    if (b[3] == 1) begin //음수인지 체크
        r_multiplier <= ~b + 1;
    end
    else begin
        r_multiplier = b;
    end

    sign <= a[3] ^ b[3]; //결과값 부호 1 이면 음수 0 이면 양수
    r_product <= 0;
    r_count <= 4;
    result <= 0;
    done <= 0;
end
LSB:begin
    r_multiplicand <= r_multiplicand; //순차회로에서 자기자신을
기억해라

    r_multiplier <= r_multiplier;
    r_count<=r_count -1;

    result <= 0;
    done <= 0;
end

ADD:
    begin
        r_product = r_multiplicand + r_product;
    end
SHIFT:
    begin
        r_multiplicand = r_multiplicand << 1;
        r_multiplier = r_multiplier >> 1;

    end

DONE:
    begin
        if (sign) begin //check if the result is negative
            result <= ~r_product+1;
        end
        else begin
            result <= r_product;
        end
    end

```

```

        done = 1;
    end
endcase
end
end

endmodule

```

```

module tb;
    reg clk, rstn, start;
    reg [3:0] a,b;

    wire [7:0]result;
    wire done;

    initial begin
        clk=0;
        forever begin
            #5 clk=!clk;
        end
    end

    mul8_sign mul8_sign(a,b,clk, rstn, start, result, done);

    initial begin
        a=-3; b=7;

        #200 $finish;
    end

    initial begin
        rstn = 0;
        #5 rstn=1;
    end

    initial begin
        start = 0;
        #20 start = 1;
    end

    initial begin
        $dumpfile("wave.vcd");
        $dumpvars(0,tb);
    end
endmodule

```



노트북에 VIVADO 가 설치가 안돼서 <https://edaplayground.com/> 를 이용하였습니다.

이 웹에는 radix 를 signed decimal 로 변경 하는 기능이 없어서.. 제가 직접 바꿔서 첨부하겠습니다. 죄송합니다.

Testbench 에서 -3 과 7 을 곱하였고 -21 이 성공적으로 나왔습니다.

Start 단계에서 multiplicand 와 multiplier 를 할당할 때 부호를 보고 음수라면 2 의 보수를 취하게 하였습니다. 또한 result 의 부호를 따지는 레지스터, `reg sign;` 을 추가하였고 start 단계에서 a, b 의 부호를 xor 하여 1 이면 음수, 0 이면 양수가 되도록 설정하였습니다. 마지막 result 에 할당할 때 음수라면 2 의 보수를 취해서 할당하도록 하였습니다.